
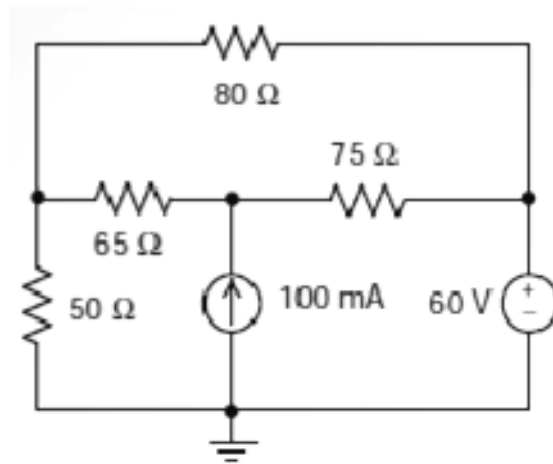


## Assignment No. 3

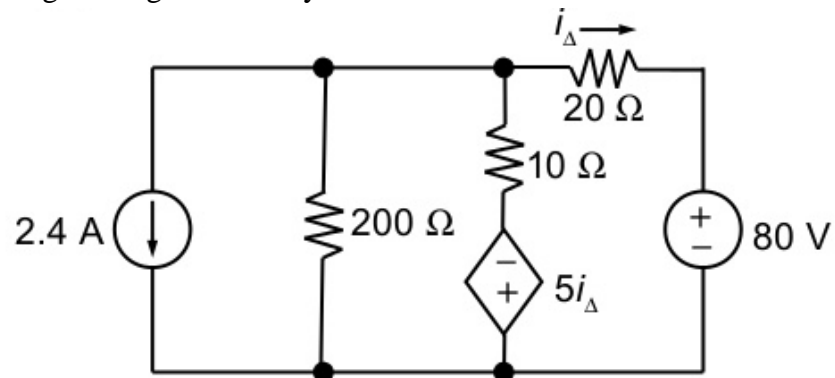
1. Find Node voltages using Node analysis:




2. Find Node voltages using nodal analysis:



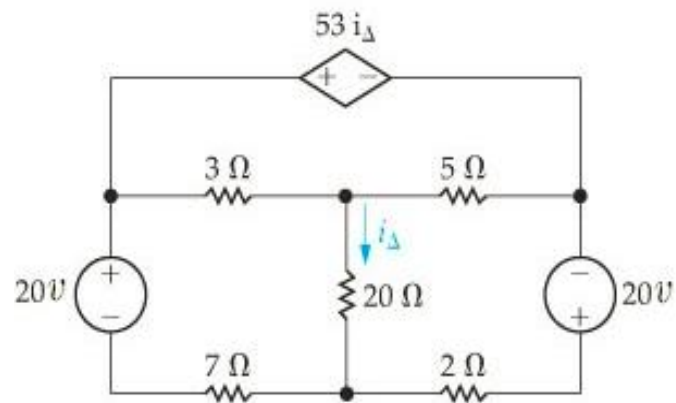3. Find Mesh currents using mesh analysis.




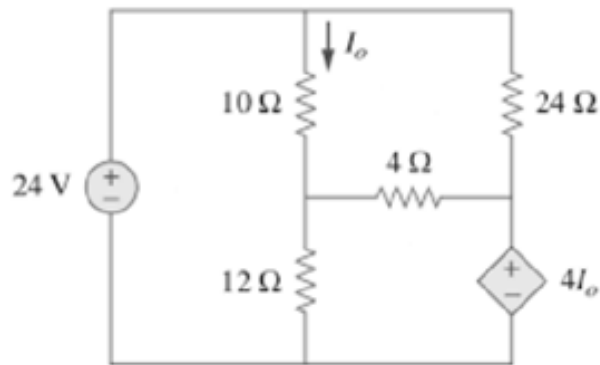4. Find Mesh currents using mesh analysis.



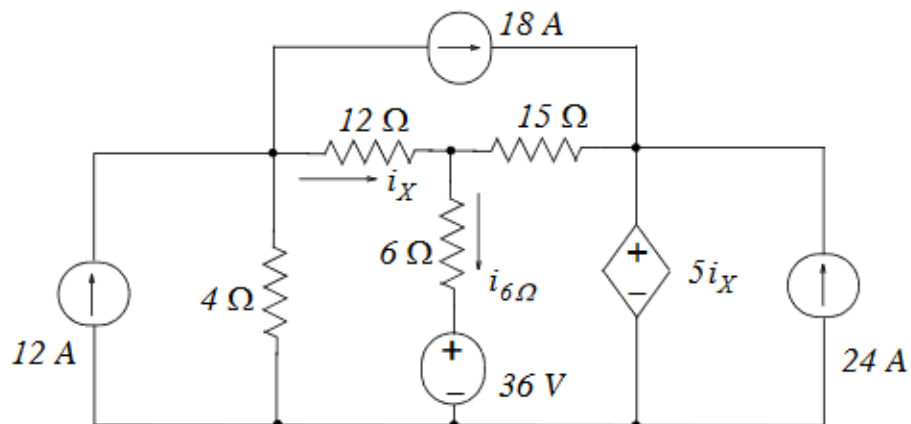
5. Find

- node voltages using Node analysis
- mesh currents using mesh analysis:




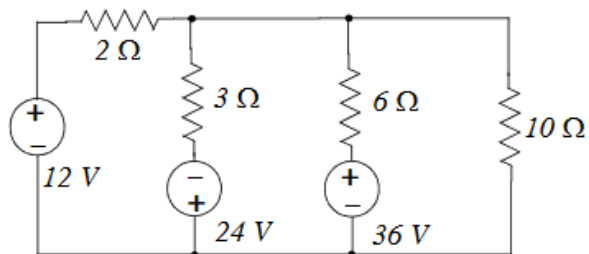6. Find


- node voltages using Node analysis
- mesh currents using mesh analysis:




7. Find voltage and energy of capacitor

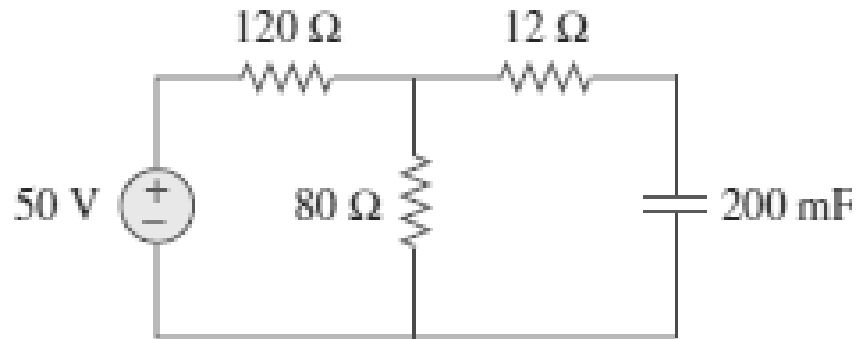

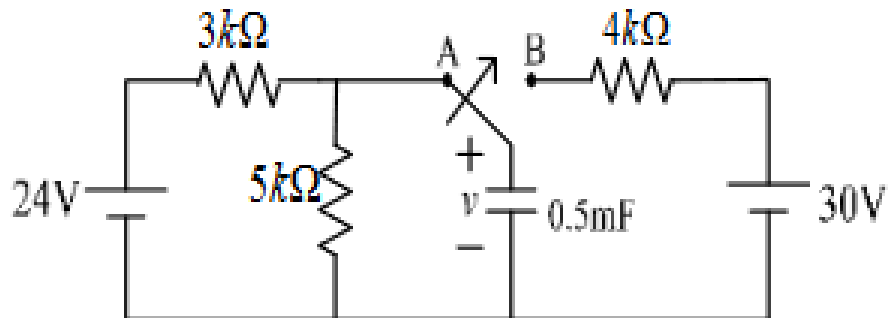
8. Find the response ' $v(t)$ ' of capacitor



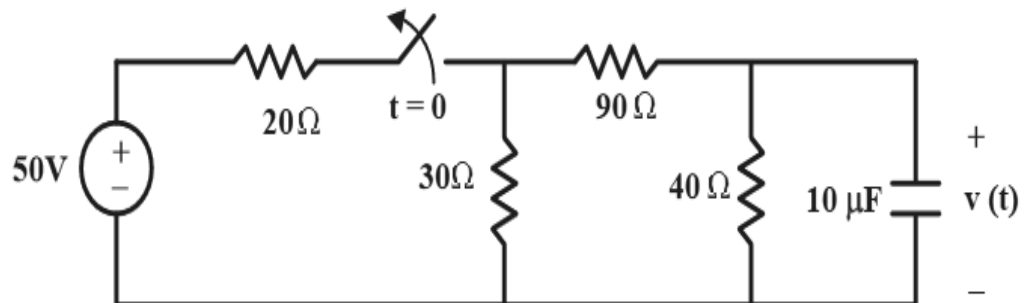9. The switch in the below circuit has been closed for a long time and is opened at  $t=0$ . Find the response ' $v(t)$ ' of the capacitor



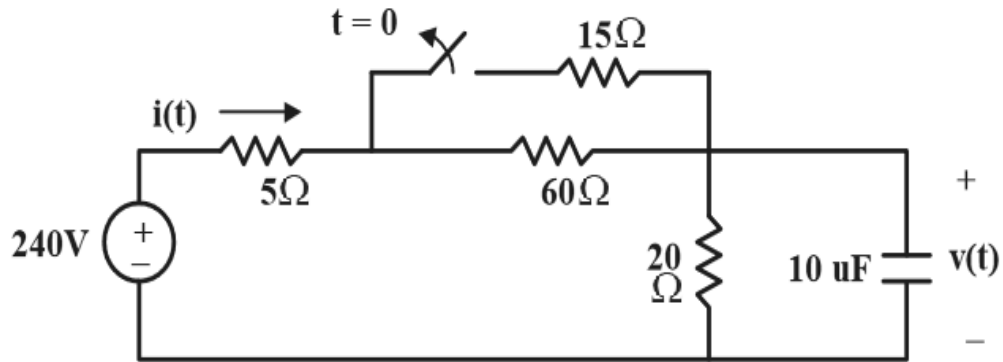
10. The switch in the below circuit has been closed for a long time and is opened at  $t=0$ . Find the response ' $v(t)$ ' and current ' $i(t)$ ' in the following circuit



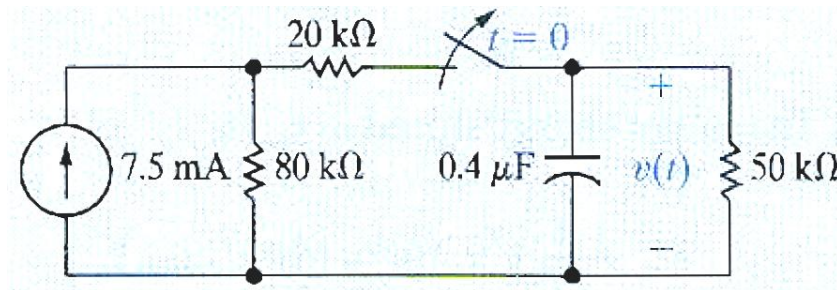11. The switch in the below circuit has been closed for a long time and is opened at  $t=0$ .


Find:

- The initial value of  $V(t)$
- The time constant for  $t > 0$
- The numerical expression for  $V(t)$  after the switch has been opened




**Answer:** (a) 200 V;  
 (b) 20 ms;  
 (c)  $200e^{-50t}$  V,  $t \geq 0$ ;

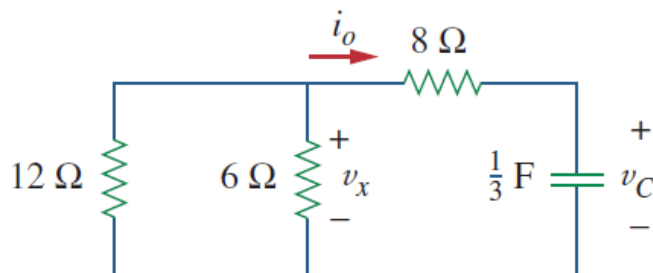12. Let  $V_C(0) = 60\text{V}$ . Determine  $V_C$ ,  $V_x$  and  $i_o$  for  $t \geq 0$ .



**Answer:**  $60e^{-0.25t}$  V,  $20e^{-0.25t}$  V,  $-5e^{-0.25t}$  A.

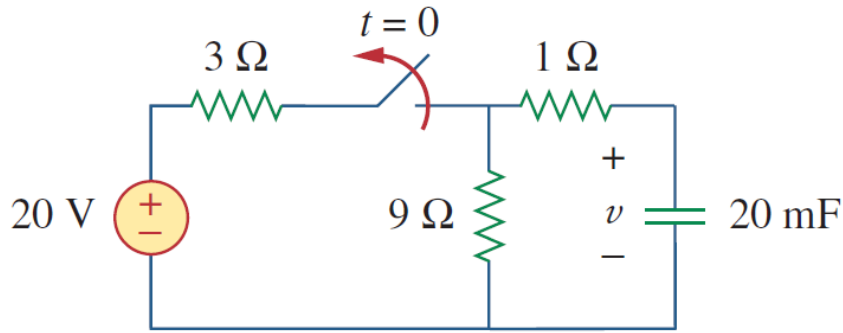
13. The switch in the circuit has been closed for a long, and it is opened at  $t = 0$ . Find  $V(t)$  for  $t \geq 0$ . Calculate the initial energy stored in the capacitor.



Answer:  $w_C(0)$  2.25 J

$$v(t) = 15e^{-5t} \text{ V}$$

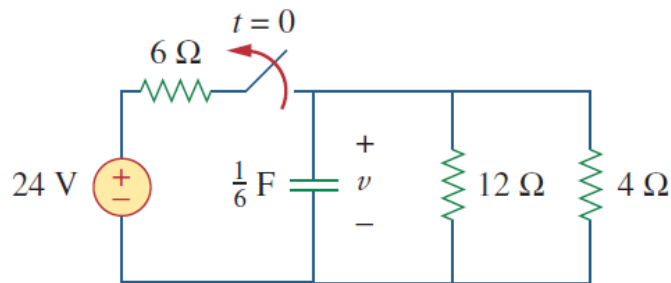14. If the switch in the below circuit open at  $t = 0$ , find  $V(t)$  for  $t \geq 0$  and also initial energy stored in the capacitor.




Answer:  $8e^{-2t} \text{ V}$ , 5.333 J.

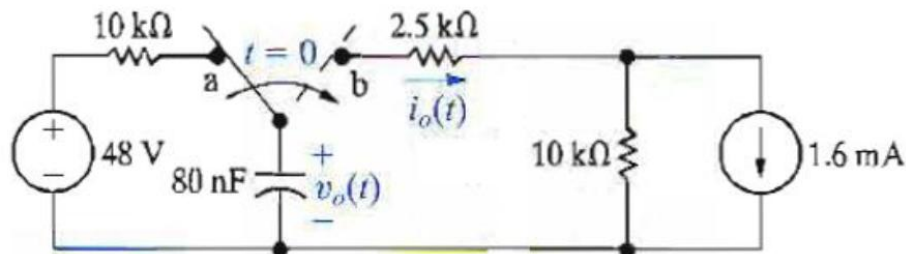15.


The switch in the circuit given below has been in position 'a' for a long time. At  $t = 0$ , the switch is moved to position 'b'.

- Find  $V_o(t)$  for  $t \geq 0$
- Find  $i_o(t)$  for  $t \geq 0^+$




Answer:  $V_o(t) = -16 + 64e^{-1000t} \text{ V}$ ,  
 $i_o(t) = 5.12e^{-1000t} \text{ mA}$

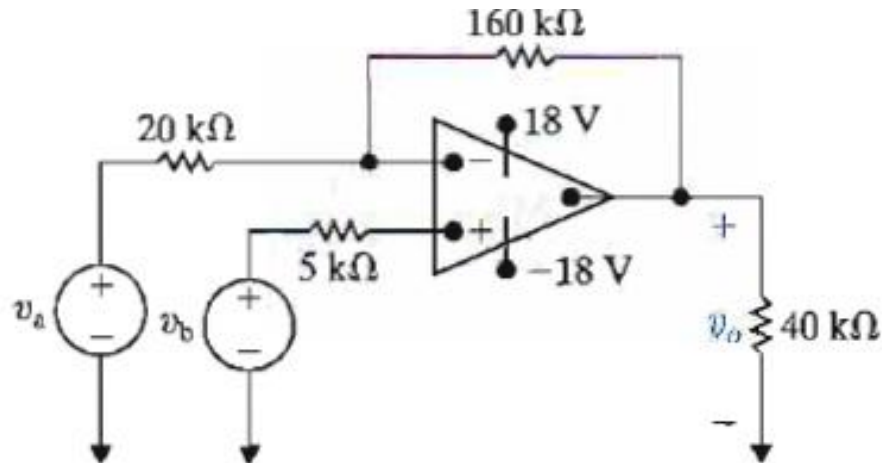16. The Op-Amp in the circuit is Ideal. Calculate  $v_o$  if  $v_a = 1.5v$  and  $v_b = 0v$ . If  $v_b = 4.5v$ , specify the range of  $v_a$  such that the amplifier does not saturate.




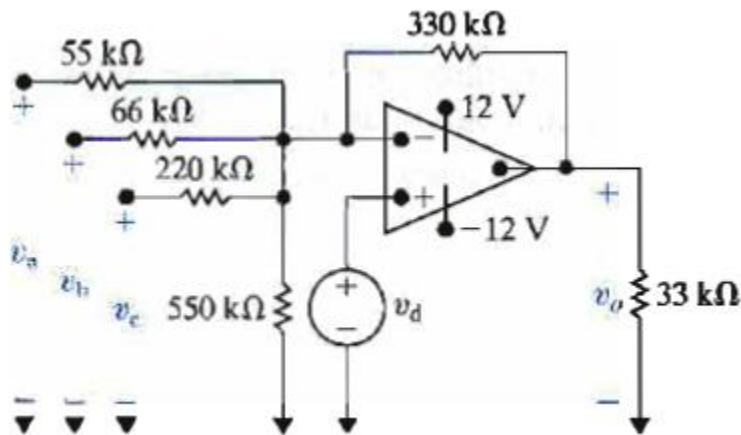17. The Op-Amp in the circuit is ideal. Find  $v_o$  if  $v_a = 16v$ ,  $v_b = 12v$ ,  $v_c = -6v$  and  $v_d = 10v$ .

If all the voltage sources except  $v_b$  retain their values, specify the range of  $v_b$  such that Op-Amp operates with in linear region.




18. Find  $i_L$  in micro amps

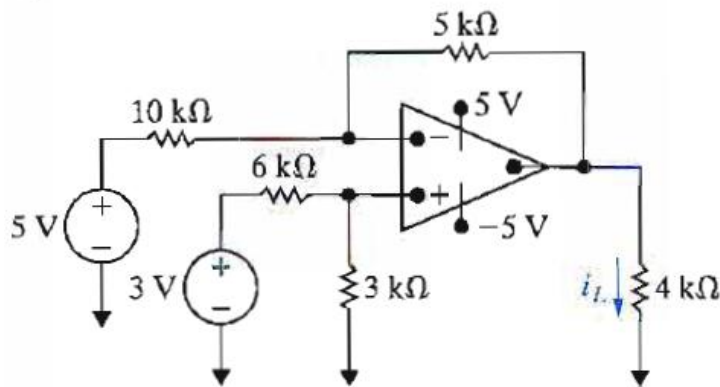

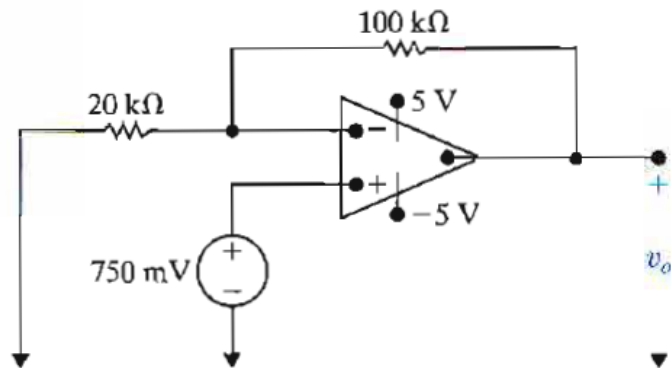19. The op amp of the following circuit is Ideal.

- What op amp configuration is this?
- Calculate  $V_o$



20. The input to the following network is given below. Find and sketch  $v_o$  if  $v_o(0) = 0$

