

Chapter 2 Diode circuits

[2-1] The zero-bias capacitance of a silicon PN junction diode is $C_{j0}=0.02\text{pF}$ and the built-in potential is $V_{bi}=0.80\text{V}$. The diode is reverse biased through a $47\text{k}\Omega$ resistor and a voltage source. For $t<0$, the applied voltage is 5V and, at $t=0$, the applied voltage drops to zero volts. Estimate the time it takes for the diode voltage to change from 5V to 1.5V . (As an approximation, use the average diode capacitance between the two voltage levels)

[2-2] The cut-in voltage of the diode shown in the circuit in Fig.E2-2 is $V_r=0.7\text{V}$. The diode is to remain biased “on” for a power supply voltage in the range $5\text{V}\leq V_{ps}\leq 10\text{V}$. The minimum diode current is to be $I_{D(\min)}=2\text{mA}$. The maximum power dissipated in the diode is to be no more than 10mW . Determine appropriate values of R_1 and R_2 .

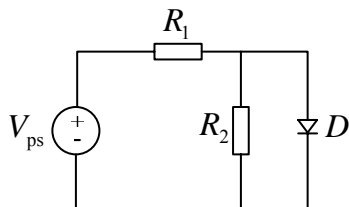


Fig.E2-2

[2-3] Assume each diode in the circuit shown in Fig.E2-3 has a cut-in voltage of $V_i=0.65\text{V}$. (a) The input voltage is $V_i=5\text{V}$. Determine the value of R_1 required such that I_{D1} is one-half the value of I_{D2} . What are the values of I_{D1} and I_{D2} ? (b) If $V_i=8\text{V}$ and $R_1=2\text{k}\Omega$, determine I_{D1} and I_{D2} .

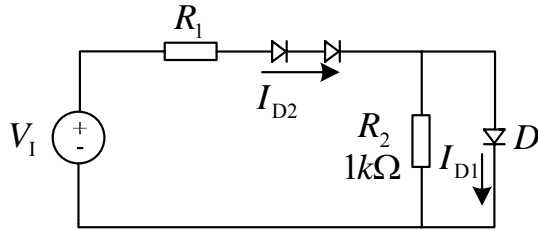


Fig.E2-3

[2-4] The diode in the circuit shown in Fig.E2-4 is biased with a constant current source I . A sinusoidal signal V_s is coupled through R_s and C . Assume that C is large so that it acts as a short circuit to the signal. (a) Find the expression of sinusoidal component of the diode voltage. (b) If $R_s=260\Omega$, find v_o/V_s , for $I=1\text{mA}$, $I=0.1\text{mA}$, and $I=0.01\text{mA}$.

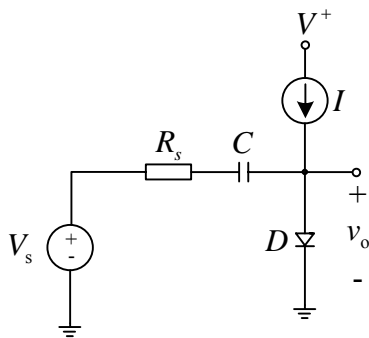


Fig.E2-4

[2-5] The full-wave rectifier circuit shown in Fig.E2-5 has an input signal whose frequency is 60Hz. The rms value of v_s is 8.5V. Assume each diode cut-in voltage is $V_F=0.7V$. (a) What is the maximum value of v_o ? (b) If $R=10\Omega$, determine the value of C such that the ripple voltage is no larger than 0.25V. (c) What must be the PIV rating of each diode?

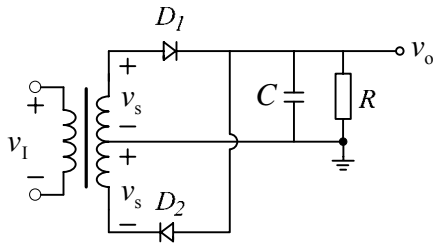


Fig.E2-5

[2-6] The circuit in Fig.E2-6 is a complementary output rectifier. Please analysis its working process (in the positive half period and negative half period of v_s). If $v_s=26\sin[2\pi(50)t]V$, sketch the output waveforms v_o^+ and v_o^- versus time, assuming $V_F=0.6V$ for each diode.

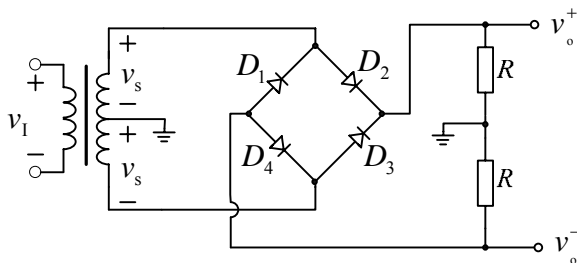


Fig.E2-6

[2-7] Consider the Zener diode circuit shown in Fig.E2-7. Assume $V_z=12\text{V}$ and $r_z=0$. (a) Calculate the Zener diode current and the power dissipated in the zener diode for $R_L = \infty$. (b) What is the value of R_L such that the current in the Zener diode is one-tenth of the current supplied by the 40V source? (c) Determine the power dissipated in the Zener diode for the conditions of part(b).

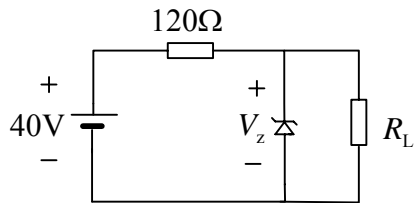


Fig. E2-7

[2-8] In the voltage regulator circuit in Fig.E2-8, let $V_i=6.3\text{V}$, $R_i=12\Omega$ and $V_z=4.8\text{V}$. The zener diode circuit is to be limited to the range $5 \leq I_z \leq 100\text{mA}$. (a) Determine the range of possible load currents and load resistances. (b) Determine the power rating required for the Zener diode and the load resistor.

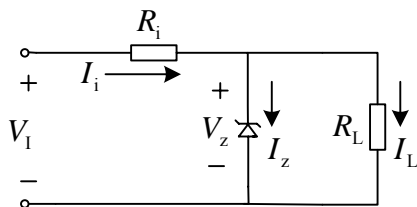


Fig.E2-8

[2-9] In the voltage regulator circuit in Fig.E2-8, $V_I=20\text{V}$, $V_Z=10\text{V}$, $R_I=222\Omega$, and $P_{Z(\max)}=400\text{mW}$. (a) Determine I_L , I_Z , and I_i , if $R_L=380\Omega$. (b) Determine the value of R_L that will establish $P_{Z(\max)}$ in the diode.

[2-10] Consider the circuit in Fig.E2-10. Let $V_r=0\text{V}$. (a) Plot v_o versus v_i over the range $-10\text{V} \leq v_i \leq +10\text{V}$. (b) Plot i_i over the same input voltage range as part(a).

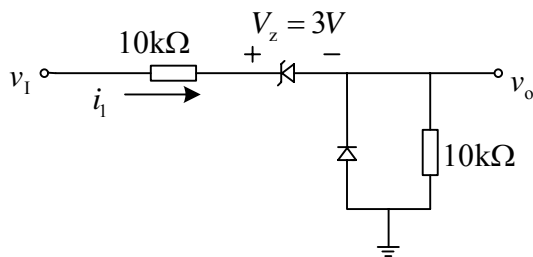


Fig.E2-10

[2-11] For the circuit in Fig.E2-11, (a) Plot v_o versus v_i for $0V \leq v_i \leq 15V$. Assume $V_T = 0.7V$. Indicate all breakpoints. (b) Plot i_D over the same range of input voltage.


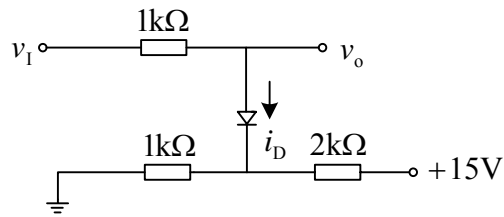


Fig.E2-11

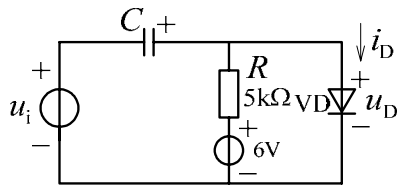[2-12] For the circuit in Fig.E2-12, $u_i = 20\sin\omega t$ (mV), $f = 1\text{kHz}$, determine the voltage u_D and current i_D , assume the capacitance C is large.



(a)

Fig. E2-12

[2-13] For the circuit in Fig.E2-13, constant current source $I=2\text{mA}$. Assume the diode voltage drop $U_D=660\text{mV}$ at 20°C , determine U_D at 50°C .

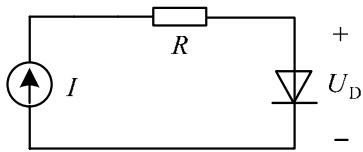


Fig. E2-13

[2-14] For the circuit in Fig.E2-14, Assume $V_r=0\text{V}$. Calculate U_Y , I_{DA} , I_{DB} , I_R under the following conditions. (a) $U_A=10\text{V}$, $U_B=0\text{V}$; (b) $U_A=6\text{V}$, $U_B=5\text{V}$; (c) $U_A=U_B=5\text{V}$.

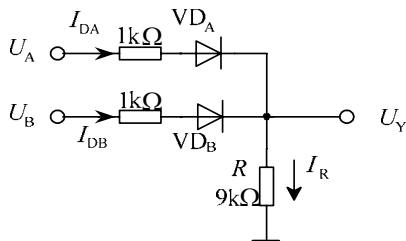


Fig.E2-14

[2-15] There are two Zener diodes, VD_{Z1} and VD_{Z2} , Zener voltage are 5.5V and 8.5V, respectively, and their forward voltage drop are all 0.5V. Design a circuit which can output stable 3V voltage.